Team 45 Report

	Ti					Bux	ALU
Instructio	m			LOAD	MEMORY	Encoder	Encoder
n	e	Control	Micro Operation	ACTIVATED	Read/Write	Output	Output
LDA A	T0		AR←PC	AR		010	,
	T1		IR←M[AR],PC←PC+1	IR	read	000	
			D0D7←Decode				
			IR(12-14), AR←IR(0-				
	T2		11), I←IR(15)	AR	_	111	
	T3	D2T3	DR←M[AR]	DR	read	000	
	T4	D2T4	AC←DR, SC←0	AC	_	100	001
DIV B	T0		AR←PC	AR	_	010	
	T1		IR←M[AR],PC←PC+1	IR		000	
			D0D7←Decode		_		
			IR(12-14), AR←IR(0-				
	T2		11), I←IR(15)	AR	read	111	
	Т3	D0T3	TR ←AC	TR	_	011	
	T4	D0T4	DR←M[AR]	DR	read	000	
	T5	D0T5	AC←DR	AC	_	100	001
	T6	D0T6	DR←TR	DR	_	101	
	T7	D0T7	AC←DR/AC,SC←0	AC	_		101
ADD C	T0		AR←PC	AR	_	010	
	T1		IR←M[AR],PC←PC+1	IR	read	000	
			D0D7←Decode				
			IR(12-14), AR←IR(0-				
	T2		11), I←IR(15)	AR	_	111	
	T3	D1T3	DR←M[AR]	DR	read	000	
			AC←AC+DR. E←Cout,				
	T4	D1T4	SC←0	AC,E	_		110
STA C	T0		AR←PC	AR	_	010	
	T1		IR←M[AR],PC←PC+1	IR	read	000	
			D0D7←Decode				
			IR(12-14), AR←IR(0-				
	T2		11), I←IR(15)	AR		111	
	T3	D3T3	$M[AR] \leftarrow AC, SC \leftarrow 0$		write	011	
LDA A	T0		AR←PC	AR	<u> </u>	010	
	T1		IR←M[AR],PC←PC+1	IR	read	000	
			D0D7←Decode				
			IR(12-14), AR←IR(0-	AB		111	
	T2	DOTO	11), I←IR(15)	AR	_	111	
	T3	D2T3	DR←M[AR]	DR	read	000	
	T4	D2T4	AC←DR, SC←0	AC	_	100	001
MUL B	T0		AR←PC	AR	_	010	

	T1		IR←M[AR],PC←PC+1	IR	read	000	
			D0D7←Decode				
			IR(12-14), AR←IR(0-				
	T2		11), I←IR(15)	AR	_	111	
	T3	D5T3	DR←M[AR]	DR	read	000	
	T4	D5T4	AC←DR*AC	AC	_		011
ADD A	T0		AR←PC	AR	_	010	
	T1		IR←M[AR],PC←PC+1	IR	read	000	
			D0D7←Decode IR(12-14), AR←IR(0-				
	T2		11), I←IR(15)	AR	_	111	
	T3	D1T3	DR←M[AR]	DR	_	000	
			AC←AC+DR. E←Cout,				
	T4	D1T4	SC←0	AC,E	_		110
STA A	T0		AR←PC	AR	_	010	
	T1		IR←M[AR],PC←PC+1	IR	_	000	
			D0D7←Decode IR(12-14), AR←IR(0-				
	T2		11), I←IR(15)	AR	_	111	
	T3	D3T3	$M[AR] \leftarrow AC, SC \leftarrow 0$		write	011	
ISZ i	T0		AR←PC	AR	_	010	
	T1		IR←M[AR],PC←PC+1	IR	read	000	
			D0D7←Decode IR(12-14), AR←IR(0-				
	T2		11), I←IR(15)	AR	_	111	
	T3	D6T3	DR←M[AR]	DR	read	000	
	T4	D6T4	DR←DR+1	DR	_		
			$M[AR] \leftarrow DR$, if(DR=0)				
	T5	D6T5	then PC←PC+1, SC←0	MR	write	100	
BUN LOP	T0		AR←PC	AR		010	
	T1		IR←M[AR],PC←PC+1	IR	read	000	
			D0D7←Decode IR(12-14), AR←IR(0-				
	T2		11), I←IR(15)	AR	<u> </u>	111	
Ì	T3	D4T3	$PC \leftarrow AR, SC \leftarrow 0$	PC	_	001	

ALU

ALU	
CONTROLS	
001	(D2T4)+(D0T5)
011	D5T5
101	D0T7
110	D1T4